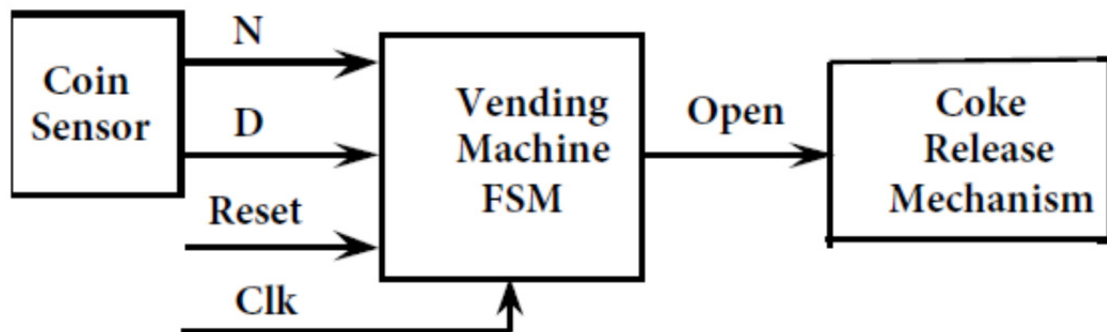



## CSE 308: Digital System Design | Homework 5 Solution

**Problem 1:** You are working as a Hardware Design Engineer at ASML in the Netherlands (just suppose!). Your boss asked you to design a vending machine with the following specifications.

- delivers a coke after 15 cents deposited
- has a single coin slot for dimes and nickels
- does not return change



Block diagram of the vending machine

 

Present State	Inputs		Next State	Output Open
	D	N		
0¢	0	0	0¢	0
	0	1	5¢	0
	1	0	10¢	0
	1	1	X	X
5¢	0	0	5¢	0
	0	1	10¢	0
	1	0	15¢	0
	1	1	X	X
10¢	0	0	10¢	0
	0	1	15¢	0
	1	0	15¢	0
	1	1	X	X
15¢	X	X	15¢	1


State diagram and state table of the vending machine

- Draw a Moore FSM for the above vending machine.
- Draw a Mealy FSM for the above vending machine.
- Implement the FSMs in (a) and (b) in Verilog.
- Show simulation results of your FSMs from (c) for the following values of clk, reset, N, and D.

Moore FSM



Mealy FSM

 


Solution:
 
## Vending Machine: Verilog (Moore FSM)

```
module vending_moore(N, D, clk, reset, open);
// Moore FSM for a vending machine
input N, D, clk, reset;
output open;
reg [1:0] state;
parameter S0=2'b00, S5=2'b01, S10=2'b10,
S15=2'b11;

// Define the sequential block
always @(posedge reset or posedge clk)
if (reset) state <= S0;
else
case (state)
S0: if (N) state <= S5;
    else if (D) state <= S10;
    else state <= S0;
S5: if (N) state <= S10;
    else if (D) state <= S15;
    else state <= S5;
S10: if (N) state <= S15;
    else if (D) state <= S15;
    else state <= S10;
S15: state <= S15;
endcase
// Define output during S3
assign open = (state == S15);
endmodule
```



## Vending Machine: Verilog (Mealy FSM)

```


module vending_mealy(N, D, clk, reset, open);
// Mealy FSM for a vending machine
input N, D, clk, reset;
output open;
reg [1:0] pstate, nstate;
reg open;
parameter S0=2'b00, S5=2'b01, S10=2'b10, S15=2'b11;

```

```


// Next state and output combinational logic
always @(N or D or pstate or reset)
    if (reset)
        begin nstate = S0; open = 0; end
    else case (pstate)
        S0: begin open = 0; if (N) nstate = S5;
            else if (D) nstate = S10;
            else nstate = S0; end
        S5: begin open = 0; if (N) nstate = S10;
            else if (D) nstate = S15;
            else nstate = S5; end
        S10: if (N | D) begin nstate = S15; open = 0; end
            else begin nstate = S10; open = 0; end
        S15: begin nstate = S0; open = 1; end
    endcase
// FF logic, use nonblocking assignments "<="
always @(posedge clk)
    pstate <= nstate;
endmodule

```

 


## Vending Machine: Simulation Results


### Moore FSM

 

### Mealy FSM

 

Problem 2:

 

- (a) Complete the Verilog code given below for the FSM shown above. The FSM has a synchronous **reset**, which forces the FSM into state S0, when **reset** is zero. State transitions occur on the positive edge of **clock**. If an invalid state is entered, the **state** should go to 2b'xx and Z should go to 2'bxx until the FSM is reset.

```

module FSM(output reg [1:0] Z, input X, clock, reset);
    reg [1:0]    state, nstate;
    parameter    S0 = 2'00, S1 = 2'b01, S2 = 2'b10;

    // implement the state register
    always @ (
                                ) begin

        end
    // implement the combinational next state and output logic
    always @ (
                                ) begin

        end
end
endmodule

```

- (b) Repeat part (a), but implement the FSM using continuous assignments for the output and flip-flop input equations, and the interface to the D flip-flop shown below for the state register.

```

module dff(q, d, clk, rst, en);

```

```

module FSM(output [1:0] Z, input X, clock, reset);
  wire [1:0] state, nstate;

  // implement the state register

  // implement the flip-flop input equations

  // implement the output equations

endmodule

```

(c) Show your state table and how you derived your input and output.

state	nstate		Z	
	X=0	X=1	X=0	X=1
00				
01				
10				
11				

(d) Complete the testbench for the FSM developed in part (b) that exhaustively tests all of the transitions shown in the state diagram. Your testbench should include a monitor statement that prints the current simulation time and all inputs and outputs when any input (except the clock) or output changes. . Your clock should have a period of 10 time units. Comment your test bench so that it is easy to see which state transitions are tested when applying a particular input value. For example, use “// S0 to S1” when testing the transition from S0 to S1.

```
module t_FSM();

// Declare your nets and variables


// Set up your clock


// Set up your monitor statement


// Instantiate your FSM


// Apply the inputs to test the transitions


endmodule
```



## Solution:

(a)

```
module FSM(output reg [1:0] Z, input X, clock, reset);
    reg [1:0]    state, nstate;
    parameter    S0 = 2'00, S1 = 2'b01, S2 = 2'b10;

    // implement the state register
    always @ (    posedge clock    ) begin
        if (~reset) state <= S0;
        else state <= nstate;
    end

    // implement the combinational next state and output logic
    always @ (    state, x    ) begin
        case (state)
            S0:    if(x) begin nstate = S1; z = 2'b01; end
                   else begin nstate = S0; z = 2'b00; end
            S1:    if(x) begin nstate = S0; z = 2'b01; end
                   else begin nstate = S2; z = 2'b00; end
            S2:    if(x) begin nstate = S1; z = 2'b11; end
                   else begin nstate = S2; z = 2'b10; end
            default:    begin nstate = 2'bxx; z = 2'bxx; end
        endcase
    end

end
endmodule
```

(b)

```
module FSM(output [1:0] Z, input X, clock, reset);
  wire [1:0] state, nstate;

  // implement the state register
  dff DFF[1:0] (state, nstate, clock, ~reset, 1'b1);

  // implement the flip-flop input equations
  assign nstate[0] = x & ~state[0];
  assign nstate[1] = ~x & (state[1] | state[0]);

  // implement the output equations
  assign z[0] = x;
  assign z[1] = state[1];

endmodule
```

(c)

state	nstate		Z	
	X=0	X=1	X=0	X=1
00	00	01	00	01
01	10	00	00	01
10	10	01	10	11
11	xx	xx	xx	xx

Equations for  $z[0]$  and  $z[1]$  derived by inspection.

Equations for  $nstate[0]$  and  $nstate[1]$  are derived by k-maps below:

K-map for  $nstate[0]$

s[1] s[0]	00	01	11	10
x	00	01	11	10
0	0	0	x	0
1	1	0	x	1

$$nstate[0] = x \ \& \ \sim state[0]$$

K-map for  $nstate[1]$

s[1] s[0]	00	01	11	10
x	00	01	11	10
0	0	1	x	1
1	0	0	x	0

$$nstate[1] = \sim x \ \& \ state[0] \ | \ \sim x \ \& \ state[1]$$

(d)

```
module t_FSM();

// Declare your nets and variables
    wire [1:0] z;
    reg x, clk, rst;

// Set up your clock
    initial begin
        clk = 0;
        forever #5 clk = ~clk;
    end
// Set up your monitor statement

    initial $monitor("%t: %b, %b, %b \n", $time, rst, x, z);


// Instantiate your FSM

    fsm DUT(z, x, clk, rst);

// Apply the inputs to test the transitions
    initial begin
        rst = 0; x = 0;           //reset to S0
        #10 rst = 1; x=0;        //S0 to S0
        #10 rst = 1; x=1;        //S0 to S1
        #10 rst = 1; x=0;        //S1 to S2
        #10 rst = 1; x=0;        //S2 to S2
        #10 rst = 1; x=1;        //S2 to S1
        #10 rst = 1; x=1;        //S1 to S0
    end

endmodule
```

 **Problem 3:** Implement the following simple Arbiter in Verilog. The Arbiter has got two request inputs and two grant outputs, as shown in the signal diagram below.



- When req\_0 is asserted, gnt\_0 is asserted
- When req\_1 is asserted, gnt\_1 is asserted
- When both req\_0 and req\_1 are asserted then gnt\_0 is asserted i.e. higher priority is given to req\_0 over req\_1.


The Arbiter has got following states.

- **IDLE:** In this state the Arbiter waits for the assertion of req\_0 or req\_1 and drives both gnt\_0 and gnt\_1 to inactive state (low). This is the default state of the Arbiter; it is entered after the reset and also during fault recovery condition.
- **GNT0:** The Arbiter enters this state when req\_0 is asserted, and remains here as long as req\_0 is asserted. When req\_0 is de-asserted, the Arbiter returns to the IDLE state.
- **GNT1:** The Arbiter enters this state when req\_1 is asserted, and remains there as long as req\_1 is asserted. When req\_1 is de-asserted, the Arbiter returns to the IDLE state.

- Draw an FSM for the above Arbiter.
- Implement the FSM in (a) in Verilog using two Always blocks.
- Implement the FSM in (a) in Verilog using single Always block.

## Solution:

(a)

 

(b)

```
1 //-----
2 // This is FSM demo program using twoalways block
3 // Design Name : fsm_using_two_always
4 // File Name   : fsm_using_two_always.v
5 //-----
6 module fsm_using_two_always (
7     clock      , // clock
8     reset      , // Active high, syn reset
9     req_0      , // Request 0
10    req_1      , // Request 1
11    gnt_0      , // Grant 0
12    gnt_1
13 );
14 //-----Input Ports-----
15 input  clock,reset,req_0,req_1;
16 //-----Output Ports-----
17 output gnt_0,gnt_1;
18 //-----Input ports Data Type-----
19 wire   clock,reset,req_0,req_1;
20 //-----Output Ports Data Type-----
21 reg     gnt_0,gnt_1;
22 //-----Internal Constants-----
23 parameter SIZE = 3 ;
24 parameter IDLE = 3'b001,GNT0 = 3'b010,GNT1 = 3'b100 ;
25 //-----Internal Variables-----
26 reg  [SIZE-1:0]      state      ;// Seq part of the FSM
27 reg  [SIZE-1:0]      next_state ;// combo part of FSM
28 //-----Code starts Here-----
29 always @ (state or req_0 or req_1)
30 begin : FSM_COMBO
31     next_state = 3'b000;
```

```

32 case(state)
33     IDLE : if (req_0 == 1'b1) begin
34         next_state = GNT0;
35     end else if (req_1 == 1'b1) begin
36         next_state = GNT1;
37     end else begin
38         next_state = IDLE;
39     end
40     GNT0 : if (req_0 == 1'b1) begin
41         next_state = GNT0;
42     end else begin
43         next_state = IDLE;
44     end
45     GNT1 : if (req_1 == 1'b1) begin
46         next_state = GNT1;
47     end else begin
48         next_state = IDLE;
49     end
50     default : next_state = IDLE;
51 endcase
52 end
53 //-----Seq Logic-----
54 always @ (posedge clock)
55 begin : FSM_SEQ
56     if (reset == 1'b1) begin
57         state <= #1 IDLE;
58     end else begin
59         state <= #1 next_state;
60     end
61 end
62 //-----Output Logic-----
63 always @ (posedge clock)
64 begin : OUTPUT_LOGIC
65     if (reset == 1'b1) begin
66         gnt_0 <= #1 1'b0;
67         gnt_1 <= #1 1'b0;
68     end
69     else begin
70         case(state)
71             IDLE : begin
72                 gnt_0 <= #1 1'b0;
73                 gnt_1 <= #1 1'b0;
74             end
75             GNT0 : begin
76                 gnt_0 <= #1 1'b1;
77                 gnt_1 <= #1 1'b0;
78             end
79             GNT1 : begin
80                 gnt_0 <= #1 1'b0;
81                 gnt_1 <= #1 1'b1;
82             end
83             default : begin
84                 gnt_0 <= #1 1'b0;
85                 gnt_1 <= #1 1'b0;
86             end
87         endcase
88     end

```

```

89 end // End Of Block OUTPUT_LOGIC
90
91 endmodule // End of Module arbiter

```

(c)

```

1 //=====
2 // This is FSM demo program using single always
3 // for both seq and combo logic
4 // Design Name : fsm_using_single_always
5 // File Name   : fsm_using_single_always.v
6 //=====
7 module fsm_using_single_always (
8     clock      , // clock
9     reset      , // Active high, syn reset
10    req_0       , // Request 0
11    req_1       , // Request 1
12    gnt_0       , // Grant 0
13    gnt_1
14 );
15 //=====Input Ports=====
16 input  clock,reset,req_0,req_1;
17 //=====Output Ports=====
18 output gnt_0,gnt_1;
19 //=====Input ports Data Type=====
20 wire   clock,reset,req_0,req_1;
21 //=====Output Ports Data Type=====
22 reg    gnt_0,gnt_1;
23 //=====Internal Constants=====
24 parameter SIZE = 3 ;
25 parameter IDLE  = 3'b001,GNT0 = 3'b010,GNT1 = 3'b100 ;
26 //=====Internal Variables=====
27 reg  [SIZE-1:0]      state      ;// Seq part of the FSM
28 reg  [SIZE-1:0]      next_state ;// combo part of FSM
29 //=====Code startes Here=====
30 always @ (posedge clock)
31 begin : FSM
32 if (reset == 1'b1) begin
33     state <= #1 IDLE;
34     gnt_0 <= 0;
35     gnt_1 <= 0;
36 end else
37     case(state)
38     IDLE : if (req_0 == 1'b1) begin
39         state <= #1 GNT0;
40         gnt_0 <= 1;
41     end else if (req_1 == 1'b1) begin
42         gnt_1 <= 1;
43         state <= #1 GNT1;
44     end else begin
45         state <= #1 IDLE;
46     end
47     GNT0 : if (req_0 == 1'b1) begin
48         state <= #1 GNT0;
49     end else begin
50         gnt_0 <= 0;

```



```
51             state <= #1 IDLE;
52         end
53     GNT1 : if (req_1 == 1'b1) begin
54         state <= #1 GNT1;
55     end else begin
56         gnt_1 <= 0;
57         state <= #1 IDLE;
58     end
59     default : state <= #1 IDLE;
60 endcase
61 end
62
63 endmodule // End of Module arbiter
```